 


Behavioral Model - Procedures (i)

- Procedures = sections of code that we know they execute sequentially
- Procedural statements = statements inside a procedure (they execute sequentially)
- e.g. another 2-to-1 mux implem:



Behavioral Model - Procedures (ii)

- Modules can contain any number of procedures
- Procedures execute in parallel (in respect to each other) and ..
- .. can be expressed in two types of blocks:
 - initial → they execute only once
 - always → they execute for ever (until simulation finishes)


"Initial" Blocks

- Start execution at sim time zero and finish when their last statement executes

```
module nothing;
```

```
    initial
```

```
        $display("I'm Groot");
```

 


Will be displayed
at sim time 0

```
    initial begin
```

```
        #50;
```
 
```
        $display("I'm Steve Rogers");
```




Will be displayed
at sim time 50

```
    end
```

```
endmodule
```

"Always" Blocks

 - Start execution at sim time zero and continue until sim finishes



Procedural Assignment with always

- Procedural assignment allows an alternative, often higher-level, behavioral description of combinational logic
- Two structured procedure statements: `initial` and `always`
- Supports richer, C-like control structures such as `if`, `for`, `while`, `case`

```
module mux_2_to_1(a, b, out,  
                  outbar, sel);  
    input a, b, sel;  
    output out, outbar;
```

Exactly the same as before.

```
    reg out, outbar;
```

Anything assigned in an `always` block must *also* be declared as `type reg` (next slide)

```
    always @ (a or b or sel)
```

Conceptually, the `always` block runs *once* whenever a signal in the **sensitivity list** changes value

```
    begin
```

```
        if (sel) out = a;  
        else out = b;
```

```
        outbar = ~out;
```

Statements within the `always` block are executed sequentially. Order matters!

```
    end
```

Surround multiple statements in a single `always` block with `begin/end`.

```
endmodule
```

Verilog Registers

- In digital design, registers represent memory elements
- Digital registers need a clock to operate and update their state on certain phase or edge
- Registers in Verilog should not be confused with hardware registers
- In Verilog, the term register (`reg`) simply means a variable that can hold a value
- Verilog registers don't need a clock and don't need to be driven like a net. Values of registers can be changed anytime in a simulation by assuming a new value to the register

Mix-and-Match Assignments


- Procedural and continuous assignments can (and often do) co-exist within a module
- Procedural assignments update the value of `reg`. The value will remain unchanged till another procedural assignment updates the variable. This is the main difference with continuous assignments in which the right hand expression is constantly placed on the left-side

```
module mux_2_to_1(a, b, out,  
                  outbar, sel);  
    input a, b, sel;  
    output out, outbar;  
    reg out;
```

```
    always @ (a or b or sel)  
    begin  
        if (sel) out = a;  
        else out = b;  
    end
```

```
    assign outbar = ~out;
```

```
endmodule
```

 

*procedural
description*

*continuous
description*

if, case Statement

- case and if may be used interchangeably to implement conditional execution within always blocks
- case is easier to read than a long string of if...else statements

```
module mux_2_to_1(a, b, out,  
                  outbar, sel);  
    input a, b, sel;  
    output out, outbar;  
    reg out;  
  
    always @ (a or b or sel)  
    begin  
        if (sel) out = a;  
        else out = b;  
    end  
  
    assign outbar = ~out;  
  
endmodule
```

```
module mux_2_to_1(a, b, out,  
                  outbar, sel);  
    input a, b, sel;  
    output out, outbar;  
    reg out;  
  
    always @ (a or b or sel)  
    begin  
        case (sel)  
            1'b1: out = a;  
            1'b0: out = b;  
        endcase  
    end  
  
    assign outbar = ~out;  
  
endmodule
```

Note: Number specification notation: <size>'<base><number>
(4'b1010 if a 4-bit binary value, 16'h6cda is a 16 bit hex number, and 8'd40 is an 8-bit decimal value)

Procedural Statements: if

```
if (expr1)
    true_stmt1;

else if (expr2)
    true_stmt2;

..
else
    def_stmt;
```

E.g. 4-to-1 mux:

```
module mux4_1(out, in, sel);
    output out;
    input [3:0] in;
    input [1:0] sel;

    reg out;
    wire [3:0] in;
    wire [1:0] sel;

    always @(in or sel)
        if (sel == 0)
            out = in[0];
        else if (sel == 1)
            out = in[1];
        else if (sel == 2)
            out = in[2];
        else
            out = in[3];
endmodule
```

Procedural Statements: case

case (expr)

item_1, .., item_n: stmt1;

item_n+1, .., item_m: stmt2;

..

default: def_stmt;

endcase

E.g. 4-to-1 mux:

```
module mux4_1(out, in, sel);
  output out;
  input [3:0] in;
  input [1:0] sel;

  reg out;
  wire [3:0] in;
  wire [1:0] sel;

  always @(in or sel)
    case (sel)
      0: out = in[0];
      1: out = in[1];
      2: out = in[2];
      3: out = in[3];
    endcase
endmodule
```

Procedural Statements: for

for (init_assignment; cond; step_assignment)
 stmt;

E.g.

```
module count(Y, start);  
output [3:0] Y;  
input start;
```

```
reg [3:0] Y;  
wire start;  
integer i;
```


```
initial  
    Y = 0;                // Vivado ok. DC_NXT not ok
```

```
always @(posedge start)  
    for (i = 0; i < 3; i = i + 1)  
        #10 Y = Y + 1;
```

```
endmodule
```

Dangers of Verilog: Incomplete Specification

Goal:

 

3-to-1 MUX

('11' input is a don't-care)

Proposed Verilog Code:

```
module maybe_mux_3to1(a, b, c,
                      sel, out);


    input [1:0] sel;
    input a,b,c;
    output out;
    reg out;

    always @(a or b or c or sel)
    begin
        case (sel)
            2'b00: out = a;
            2'b01: out = b;
            2'b10: out = c;
        endcase
    end
endmodule
```


Is this a 3-to-1 multiplexer?

Language Directed View

 - Inferring combinational logic
 - every combination of inputs produces an output
 - every execution path performs an assignment to every signal



 - Inferring sequential logic
 - a signal is not assigned in some execution path




remember the value, i.e., storage

Incomplete Specification Infers Latches

```
module maybe_mux_3to1(a, b, c,  
                      sel, out);  
  
    input [1:0] sel;  
    input a,b,c;  
    output out;  
    reg out;  
  
    always @(a or b or c or sel)  
    begin  
        case (sel)  
            2'b00: out = a;  
            2'b01: out = b;  
            2'b10: out = c;  
        endcase  
    end  
endmodule
```

if out is not assigned
during any pass through
the always block, then **the
previous value must be
retained!**

Synthesized Result:

 

- Latch memory “latches” old data when G=0 (we will discuss latches later)
- In practice, we almost *never* intend this

Avoiding Incomplete Specification

- Precede all conditionals with a default assignment for all signals assigned within them...

```
always @(a or b or c or sel)
begin
    out = 1'bx;
    case (sel)
        2'b00: out = a;
        2'b01: out = b;
        2'b10: out = c;
    endcase
end
endmodule
```

```
always @(a or b or c or sel)
begin
    case (sel)
        2'b00: out = a;
        2'b01: out = b;
        2'b10: out = c;
        default: out = 1'bx;
    endcase
end
endmodule
```

- ...or, fully specify all branches of conditionals and assign all signals from all branches

- For each if, include else
- For each case, include default

The Sequential always Block


- Edge-triggered circuits are described using a sequential always block

Combinational

```
module combinational(a, b, sel,
                    out);

    input a, b;
    input sel;
    output out;
    reg out;

     always @ (a or b or sel)
    begin
        if (sel) out = a;
        else out = b;
    end
endmodule
```




Sequential

```
module sequential(a, b, sel,
                 clk, out);

    input a, b;
    input sel, clk;
    output out;
    reg out;

     always @ (posedge clk)
    begin
        if (sel) out <= a;
        else out <= b;
    end
endmodule
```



Blocking vs. Nonblocking Assignments

- Verilog supports two types of assignments within `always` blocks, with subtly different behaviors.
- **Blocking assignment:** evaluation and assignment are immediate

```
always @ (a or b or c)
begin
```

```
  x = a | b;           1. Evaluate  $a | b$ , assign result to x
```

```
  y = a ^ b ^ c;       2. Evaluate  $a^b^c$ , assign result to y
```

```
  z = b & ~c;          3. Evaluate  $b \& (\sim c)$ , assign result to z
```

```
end
```

- **Nonblocking assignment:** all assignments deferred until all right-hand sides have been evaluated (end of simulation timestep)

```
always @ (a or b or c)
begin
```

```
  x <= a | b;           1. Evaluate  $a | b$  but defer assignment of x
```

```
  y <= a ^ b ^ c;       2. Evaluate  $a^b^c$  but defer assignment of y
```

```
  z <= b & ~c;          3. Evaluate  $b \& (\sim c)$  but defer assignment of z
```

```
end                     4. Assign x, y, and z with their new values
```

- Sometimes, as above, both produce the same result. Sometimes, not!


Blocking and Nonblocking: how to predict behavior?

1. A procedure takes zero time to schedule events.
2. All statements are executed sequentially.
3. Blocking assignments take effect immediately.
4. Nonblocking assignments take effect after the delta delay.
5. A procedure executes only when an event occurs on the signals in the sensitivity list.

Blocking vs. Nonblocking


```
always @ (a, b, c)
begin
  x = a & b;
  y = x | c;
end
```

```
always @ (a, b, c)
begin
  x <= a & b;
  y <= x | c;
end
```

 

Assignment Styles for Sequential Logic

*Flip-Flop Based
Digital Delay
Line*


 


- Will nonblocking and blocking assignments both produce the desired result?

```
module nonblocking(in, clk, out);  
  input in, clk;  
  output out;  
  reg q1, q2, out;  
  always @ (posedge clk)  
  begin  
    q1 <= in;  
    q2 <= q1;  
    out <= q2;  
  end  
endmodule
```

```
module blocking(in, clk, out);  
  input in, clk;  
  output out;  
  reg q1, q2, out;  
  always @ (posedge clk)  
  begin  
    q1 = in;  
    q2 = q1;  
    out = q2;  
  end  
endmodule
```


Assignment Styles for Sequential Logic

  

Use Nonblocking for Sequential Logic


```
always @ (posedge clk)
begin
    q1 <= in;
    q2 <= q1;
    out <= q2;
end
```

 “At each rising clock edge, $q1$, $q2$, and out simultaneously receive the old values of in , $q1$, and $q2$.”



```
always @ (posedge clk)
begin
    q1 = in;
    q2 = q1;
    out = q2;
end
```

 “At each rising clock edge, $q1 = in$.
After that, $q2 = q1 = in$.
After that, $out = q2 = q1 = in$.
Therefore $out = in$.”




- Blocking assignments do not reflect the intrinsic behavior of multi-stage sequential logic
- **Guideline: use nonblocking assignments for sequential always blocks**

Use Blocking for Combinational Logic

Blocking Behavior

	a	b	c	x	y
(Given) Initial Condition	1	1	0	1	1
a changes; always block triggered	0	1	0	1	1
x = a & b;	0	1	0	0	1
y = x c;	0	1	0	0	0

 

```

module blocking(a,b,c,x,y);
  input a,b,c;
  output x,y;
  reg x,y;

  always @ (a or b or c)
  begin
    x = a & b;
    y = x | c;
  end
endmodule
  
```

Nonblocking Behavior

	a	b	c	x	y	Deferred
(Given) Initial Condition	1	1	0	1	1	
a changes; always block triggered	0	1	0	1	1	
x <= a & b;	0	1	0	1	1	x<=0
y <= x c;	0	1	0	1	1	x<=0, y<=1
Assignment completion	0	1	0	0	1	

```


module nonblocking(a,b,c,x,y);
  input a,b,c;
  output x,y;
  reg x,y;

  always @ (a or b or c)
  begin
    x <= a & b;
    y <= x | c;
  end
endmodule
  
```



- Nonblocking and blocking assignments will synthesize correctly. Will both styles simulate correctly?
- Nonblocking assignments do not reflect the intrinsic behavior of multi-stage combinational logic
- While nonblocking assignments can be hacked to simulate correctly (expand the sensitivity list), it's not elegant
- **Guideline: use blocking assignments for combinational always blocks**

Flip-flop Verilog code
 
```
always @ (posedge clk)
begin
    q <= d;
end
```




Blocking vs. Nonblocking: flip-flop

  

Blocking vs. Nonblocking: flip-flop
 
```
always @ (posedge clk)
begin
    v = x & y;
    d1 <= v ~& z;
end;
```



Blocking vs. Nonblocking: flip-flop

```
always @ (posedge clk)
begin
    s <= x & y;
    d2 <= s ~& z;
end;
```

